

BANGLADESH UNIVERSITY OF ENGINEERING AND
TECHNOLOGY

CSE306

COMPUTER ARCHITECTURE SESSIONAL

Assignment - 2

Implementation of 16 bit Floating Point Adder

Submitted By:

Group: A1 - 1

Kowshic Roy

(S201705001)

Sheikh Azizul Hakim

(S201705002)

Mahdi Hasnat Siyam

(S201705003)

Saiful Islam

(S201705006)

Khandokar Md. Rahat

Hossain

(S201705024)

Department of CSE

Submitted To:

Abu Wasif

Assistant Professor

Madhusudan Basak

Assistant Professor

T. M. Tariq Adnan

Lecturer

Department of CSE

Date of Submission : May 30, 2021

1 Introduction

Floating point adder is a combinatorial circuit that performs the addition operation of two signed floating point numbers. In this assignment, we had to design a 16-bit floating point adder circuit which takes two 16-bit floating point numbers as inputs and provides their sum, another 16-bit floating point number, as the output.

2 Problem Specification

Each 16-bit number would be represented as:

Sign 1-bit	Exponent 4-bit				Fraction 11-bit										
s	e_3	e_2	e_1	e_0	f_{10}	f_9	f_8	f_7	f_6	f_5	f_4	f_3	f_2	f_1	f_0
S	E				F										

Table 1: 16 bit representation of numbers

Here we assume that the numbers are in normalized form and their exponents are biased with $B = 2^{4-1} - 1 = 7$. Hence, a number N having representation SEF is equal to

$$N = (-1)^S \times 1.F \times 2^{E-7}$$

Let the two numbers be denoted by $N_a = S_a E_a F_a$ and $N_b = S_b E_b F_b$. The task is to do the summation and output the result in truncated normalized form in the same 16 bit representation($S_r E_r F_r$). IEEE754 standard has some special values for representing infinity, sub-normalized numbers. These were also taken care of. Again, the circuit has underflow and overflow flags to indicate underflow or overflow occurrence respectively.

3 Methodology

The workflow of the FP adder can be divided into several segments which are mentioned below :

1. Sorting and Reconstructing the numbers

If $E_a < E_b$, we swapped the numbers so the N_a always carries the maximum exponent value.

Here $E_r = E_a$ is our initial resulting exponent which may or may not be changed later.

Reconstruction method: The implicit 1 (left of radix point) in our representation was introduced before the 11 bit fraction part(1F) which is our mantissa(M). Now our mantissa is of 12 bits. To make it of 16 bits, we introduced two zeroes before and after the mantissa M . So, finally $M = 001F00$.

Two mantissas M_a and M_b were reconstructed using *Reconstruction* method mentioned above.

2. Making the exponents equal

We right shifted the mantissa M_b by $(E_a - E_b)$.

3. Adding the Mantissa's

We calculated the resulting Mantissa as well as resulting sign by passing two Mantissas M_a and M_b along with their signs S_a and S_b to a 16 bit modified ALU.

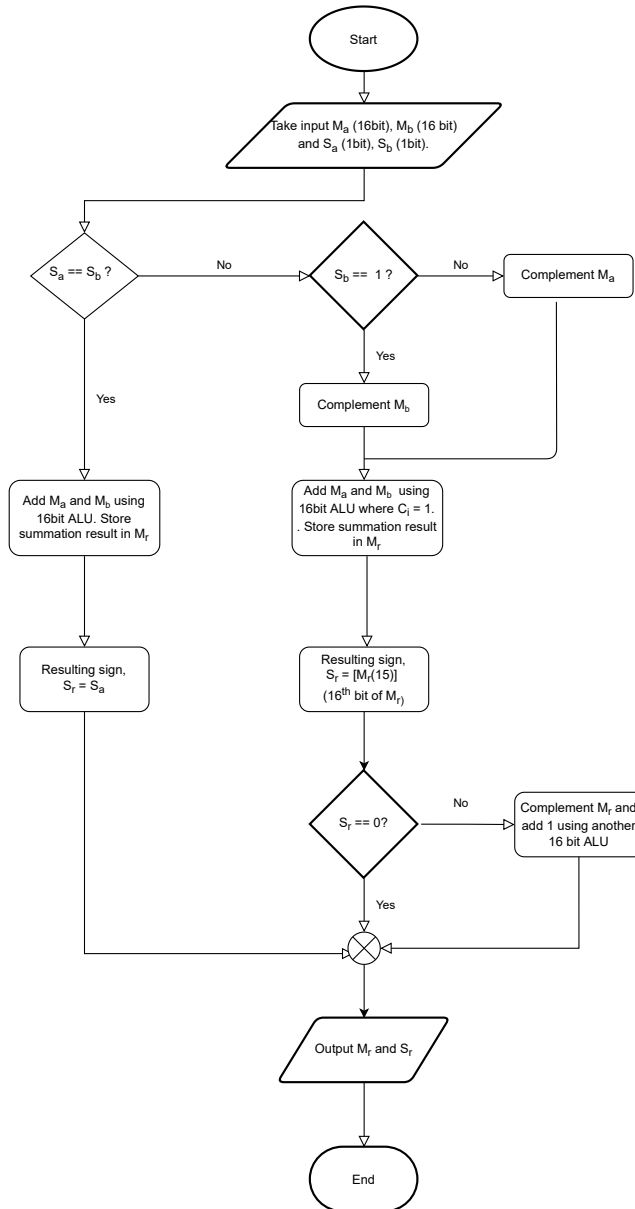


Figure 1: Flowchart of the Modified ALU

4. Normalizing the resulting Mantissa

We normalized M_r and adjusted E_r if necessary. We also checked whether overflow or underflow had occurred.

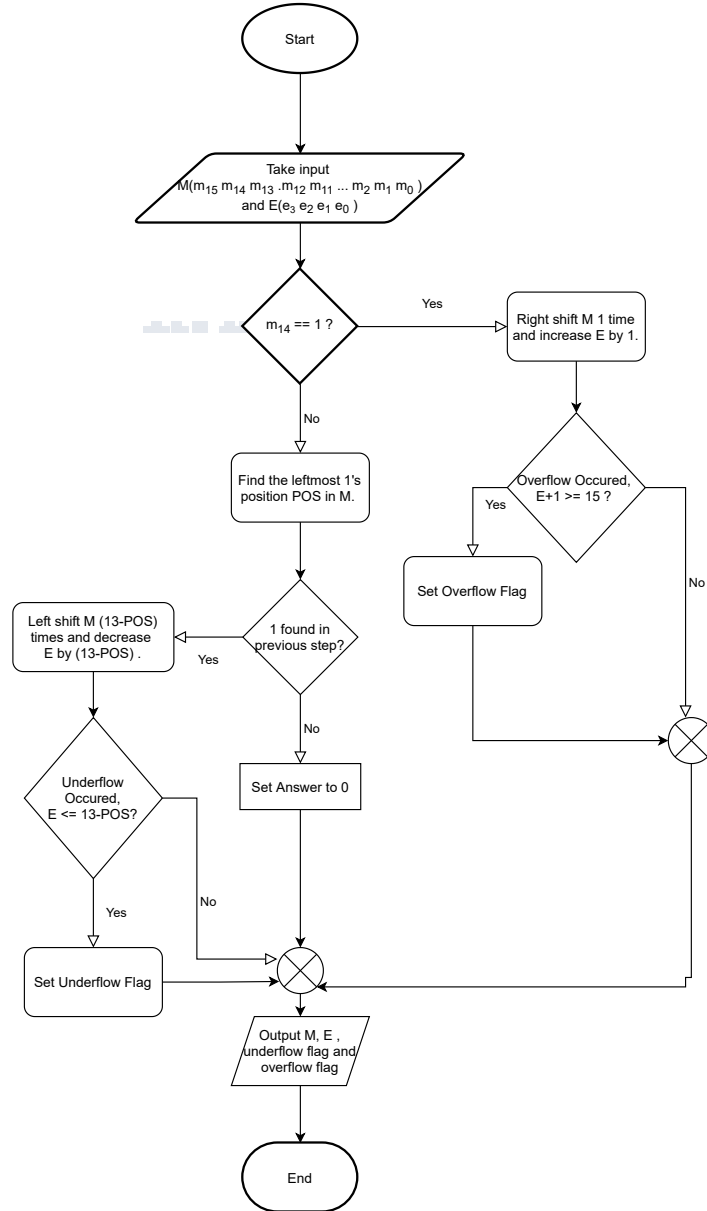


Figure 2: Flowchart of the Normalizer

5. Output

In case of overflow or underflow, corresponding flag bits were set.

In other cases,

sign bit as S_r ,

exponent as E_r ,

fraction as $m_{12}m_{11}m_{10} \dots m_4m_3m_2$ of M_r .

Overall Logic Flow Diagram :

Here we present a block diagram of the whole process. Abstraction for modified ALU and normalizer were used to keep things simple.

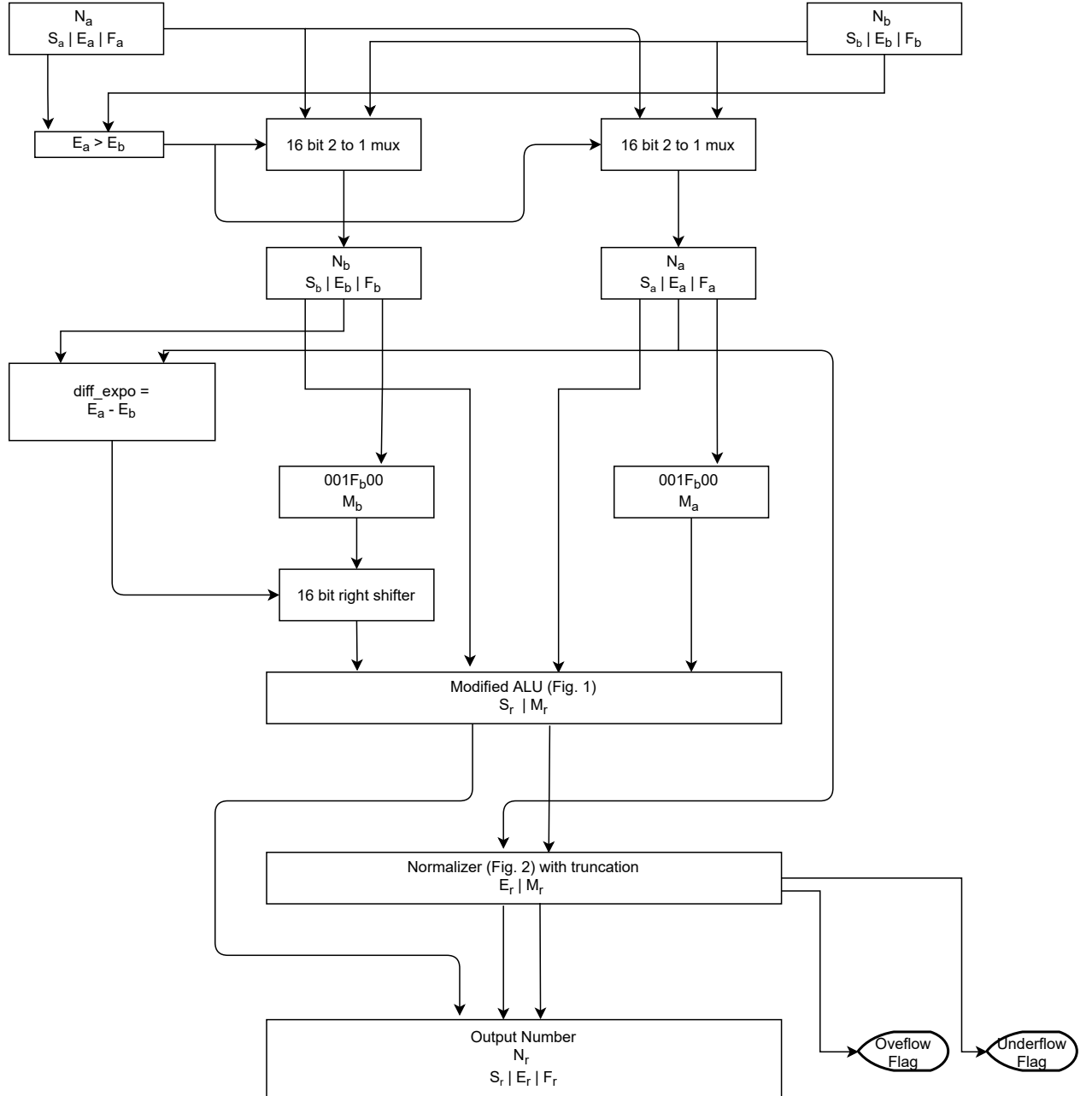


Figure 3: High level view of implementation of the FP Adder

4 Implementation

4.1 Logic Gate Diagrams

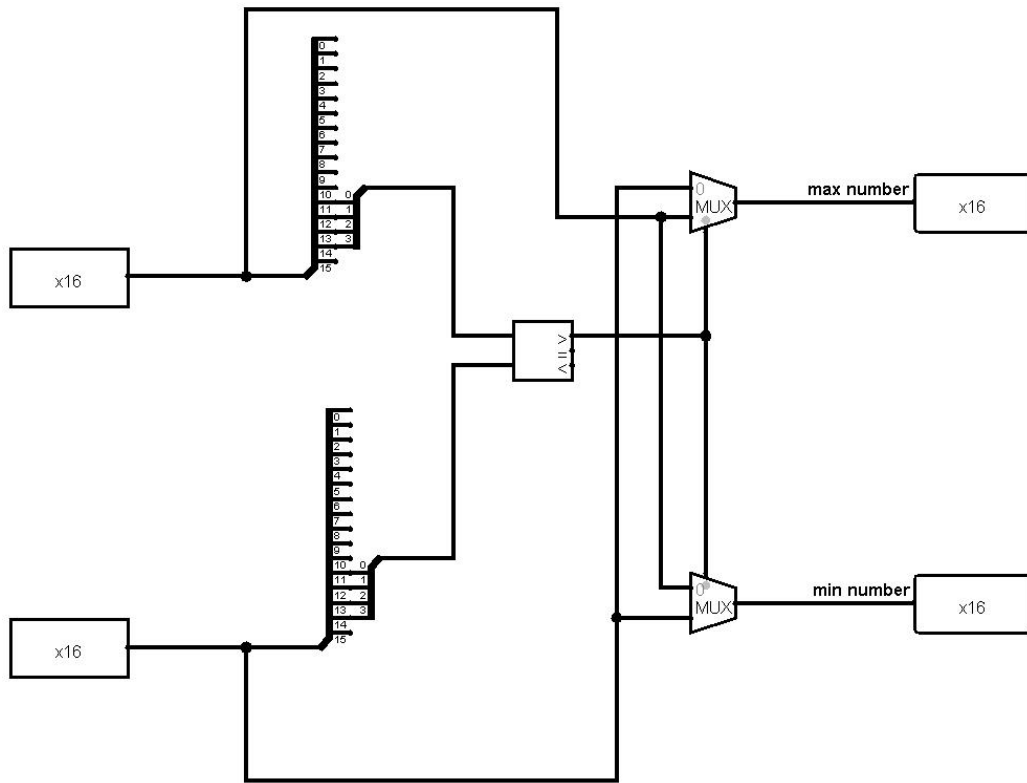


Figure 4: Gate Diagram of the input sorter

 


Figure 5: Gate Diagram of the Floating point Decoder

 


Figure 6: Gate Diagram of the Modified ALU

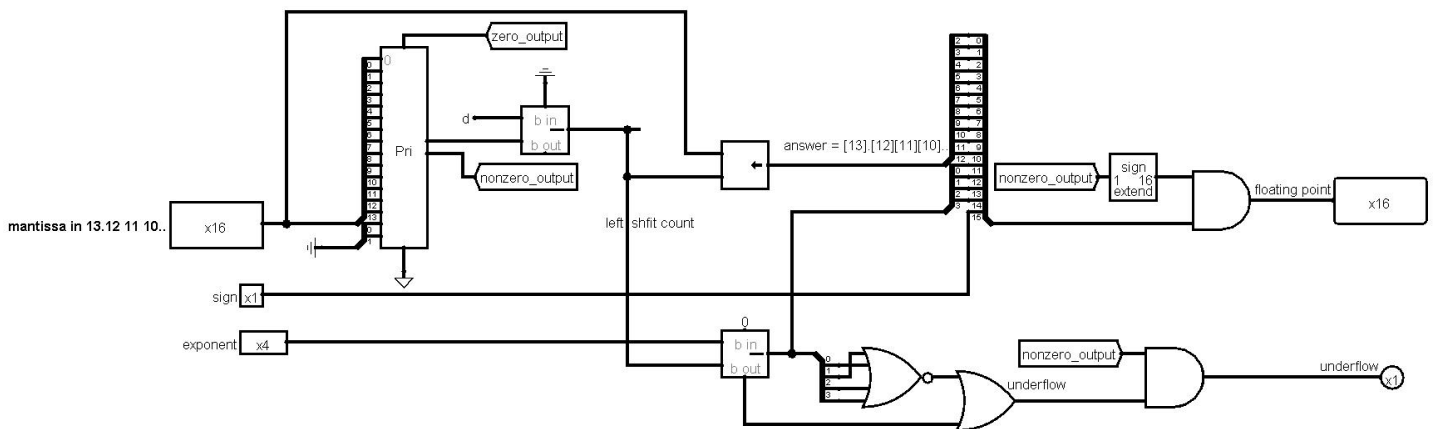


Figure 7: Gate Diagram of the Normalizer

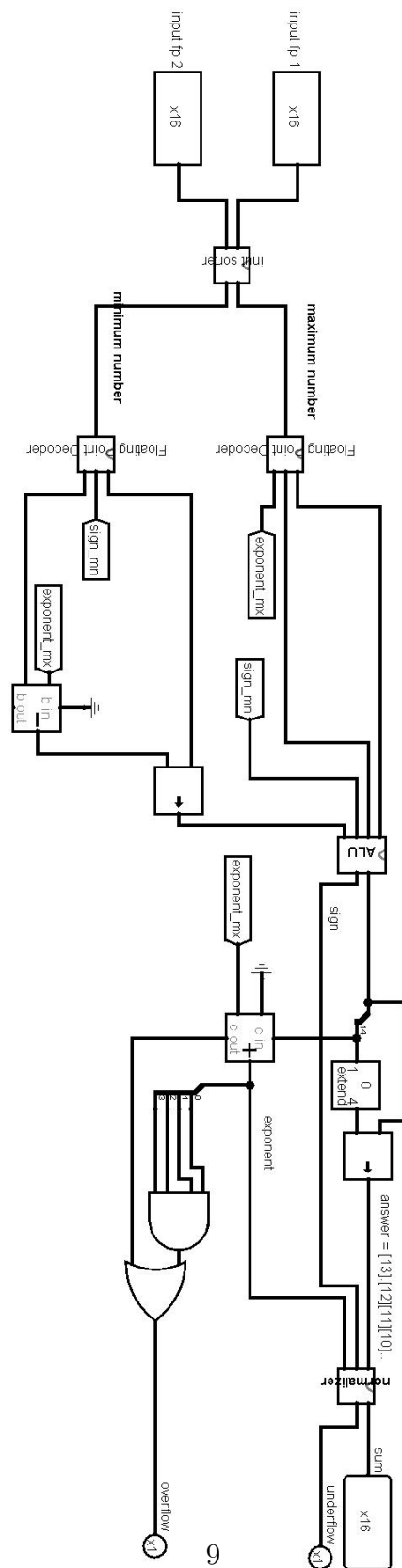


Figure 8: Gate Diagram of the FP Adder

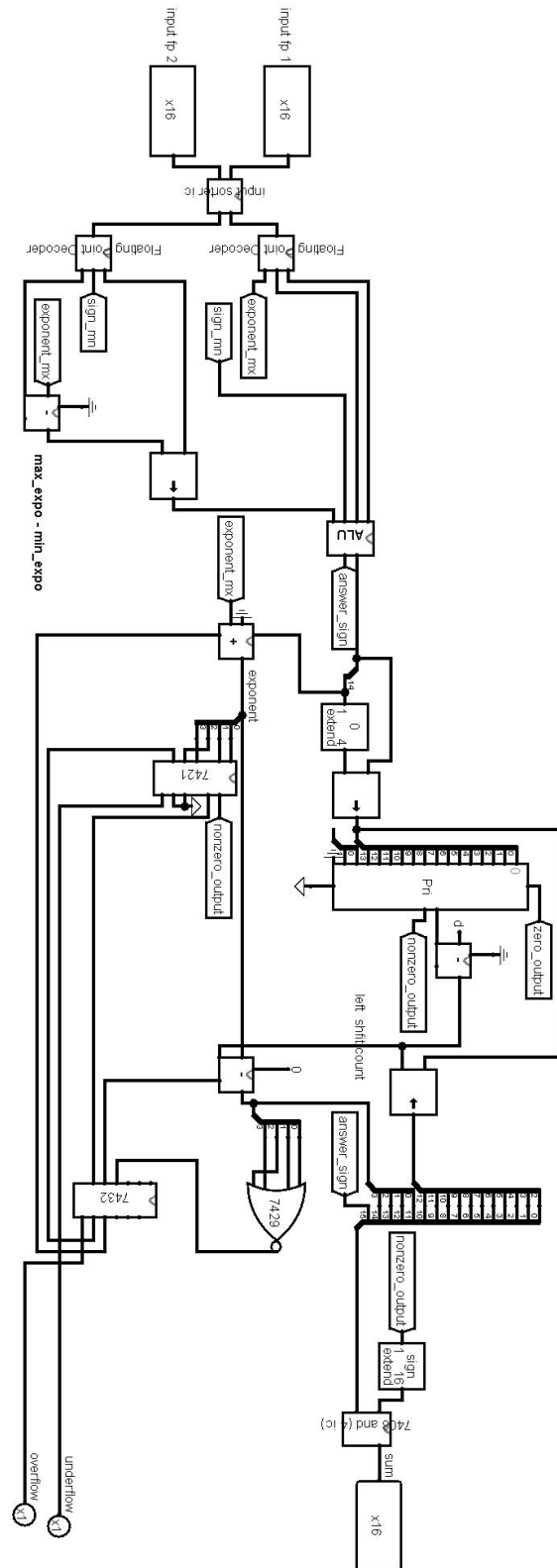


Figure 11: IC Diagram of the FP Adder

5 Block Diagram

 


Figure 12: Block Diagram of Floating Point Adder

6 IC count

Part Number	Description	Count
7485	4-bit Magnitude Comparator	1
74157	Quad 2-Input Multiplexer	8
74181	4-bit Slice Arithmetic Logic Unit (ALU)	3
74283	4-Bit Binary Adder	9
7486	Quad 2-Input XOR Gate	13
7408	Quad 2-Input AND Gate	5
7421	Dual 4-Input AND Gate	1
7432	Quad 2-Input OR Gate	1
7429	Dual 4-Input NOR Gate	1
	16-Line to 4-Line Priority Encoder	1
	16 bit Logical Shifter	3
Total		46

Table 2: List of ICs used in the simulation

7 Simulator Details

In this assignment we used **Logisim** v2.7.1, which is an open-source software for simulating digital circuits. More information about this software can be found at: <http://www.cburch.com/logisim/index.html>

8 Discussion

In this experiment, we designed a floating point adder to facilitate a subset of operations supported by IEEE754. Our circuit is only valid for normalized inputs but it can be easily extended for sub-normalized numbers by simply adding two more 4-input OR gate (one 744072 IC unit).

The focus of our design was on the efficiency of design and minimization of ICs used. For example, two “8-line to 3-line priority encoder (IC 74148)” can be concatenated to make “16-line to 4-line priority encoder”. We can also implement the 16-bit logical shifter with 16 “16-line to 1-line multiplexer”. But we used logisim’s default shifter and priority encoder for the simplicity of the design.